Performance Evaluation of a Novel Ternary CNTFET SRAM Cell

Pramod Srinivasan

BITS-Pilani

29 January 2015
Shillong

Overview

Emerging Nanotechnologies - Post-CMOS Alternatives

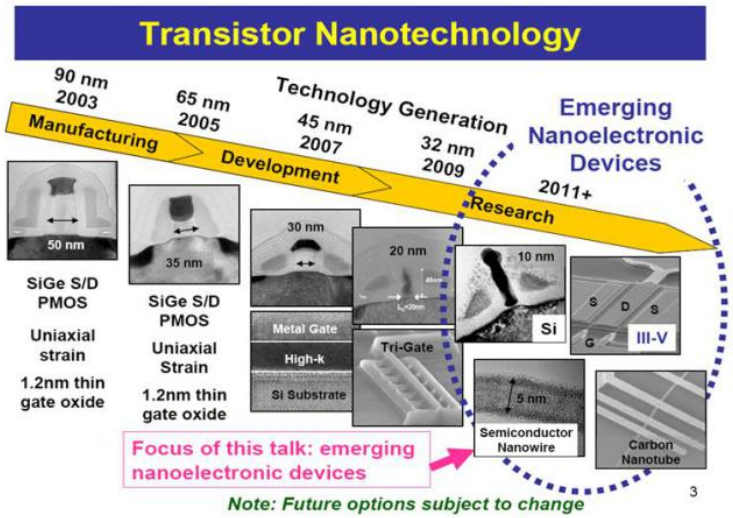

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

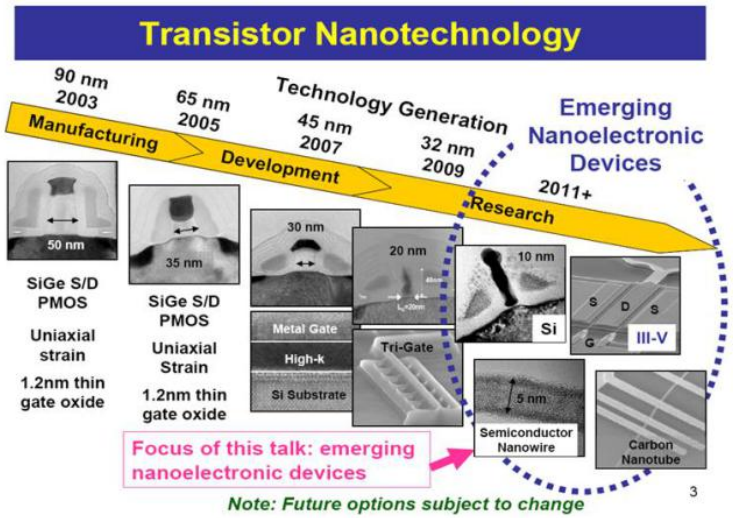

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

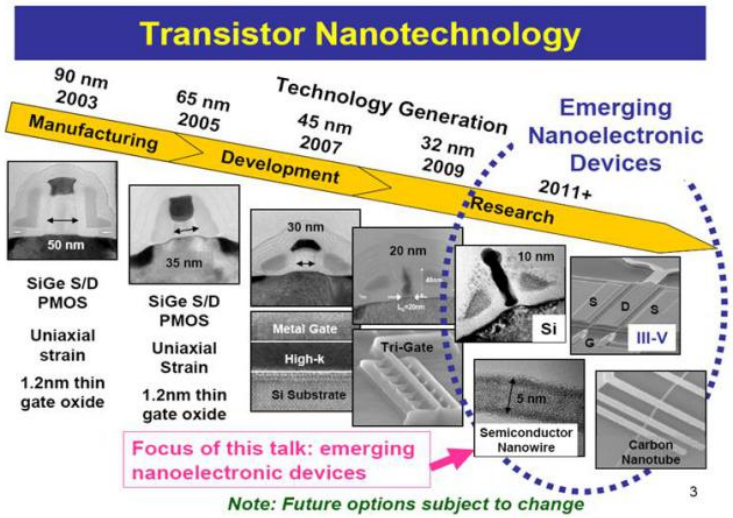

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

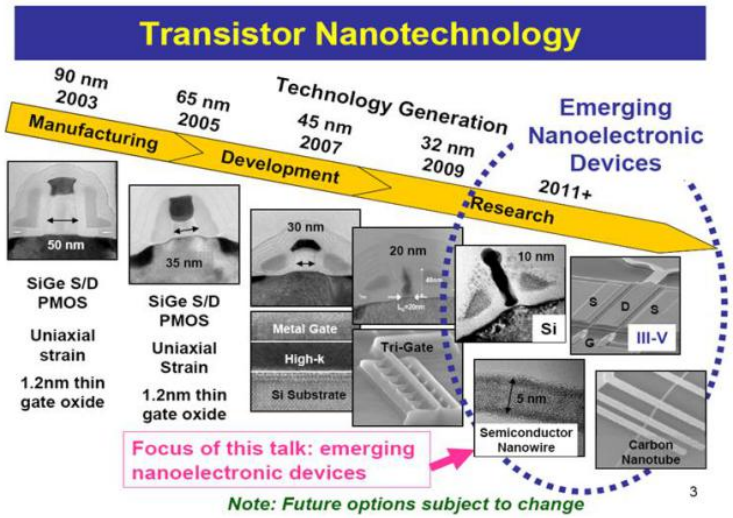

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

CNTFET as the best alternative to CMOS

- Faster switching speeds and low power
- Bistability gives well defined on and off states
- P and N type CNTFETs of same size having same mobility
- Ballistic Nature suitable for high frequency operations -**100GHz**

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

CNTFET as the best alternative to CMOS

- Faster switching speeds and low power
- Bistability gives well defined on and off states
- P and N type CNTFETs of same size having same mobility
- Ballistic Nature suitable for high frequency operations -**100GHz**

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

CNTFET as the best alternative to CMOS

- Faster switching speeds and low power
- Bistability gives well defined on and off states
- P and N type CNTFETs of same size having same mobility
- Ballistic Nature suitable for high frequency operations -**100GHz**

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Emerging Nanotechnologies - Post-CMOS Alternatives

CNTFET as the best alternative to CMOS

- Faster switching speeds and low power
- Bistability gives well defined on and off states
- P and N type CNTFETs of same size having same mobility
- Ballistic Nature suitable for high frequency operations -**100GHz**

Critical Challenges in nanoscale

- Variations in I-V characteristics
- Reduced gate control
- Larger process variations

Heralding the Post-CMOS Era

BBC Science,September 2013

First computer made of carbon nanotubes is unveiled at Stanford

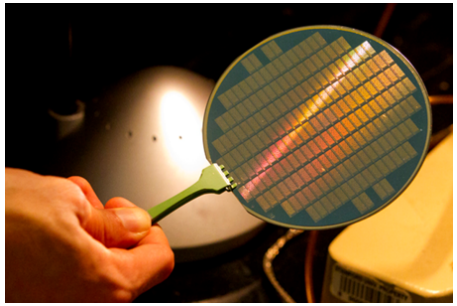

IEEE Spectrum,Jan 2014

Nanotubes Could Solve Overheating Problem for Next-Gen Computer Chips

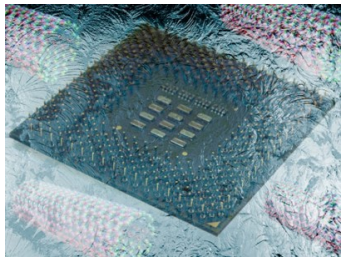

PhysicsWorld,Mar 2013

Nanotube transistors detect cancer biomarkers

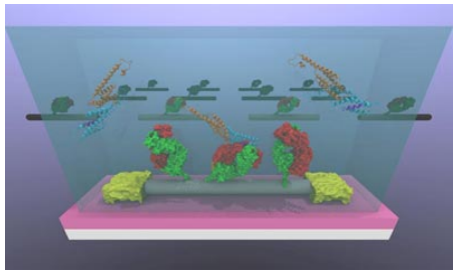

Ternary Logic with CNTFETs

- Reduces chip area
- Reduces complexity of interconnect with enhancing their information content
- Attains simplicity and energy efficiency in designing of digital circuits

Best way of designing is **multiple-threshold method** which can be achieved by utilizing **different diameters of Nanotubes**

Ternary Logic with CNTFETs

- Reduces chip area
- Reduces complexity of interconnect with enhancing their information content
- Attains simplicity and energy efficiency in designing of digital circuits

Best way of designing is **multiple-threshold method** which can be achieved by utilizing **different diameters of Nanotubes**

Ternary Logic with CNTFETs

- Reduces chip area
- Reduces complexity of interconnect with enhancing their information content
- Attains simplicity and energy efficiency in designing of digital circuits

Best way of designing is **multiple-threshold method** which can be achieved by utilizing **different diameters of Nanotubes**

Ternary Logic with CNTFETs

- Reduces chip area
- Reduces complexity of interconnect with enhancing their information content
- Attains simplicity and energy efficiency in designing of digital circuits

Best way of designing is **multiple-threshold method** which can be achieved by utilizing **different diameters of Nanotubes**

Ternary Logic with CNTFETs

- Reduces chip area
- Reduces complexity of interconnect with enhancing their information content
- Attains simplicity and energy efficiency in designing of digital circuits

Best way of designing is **multiple-threshold method** which can be achieved by utilizing **different diameters of Nanotubes**

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

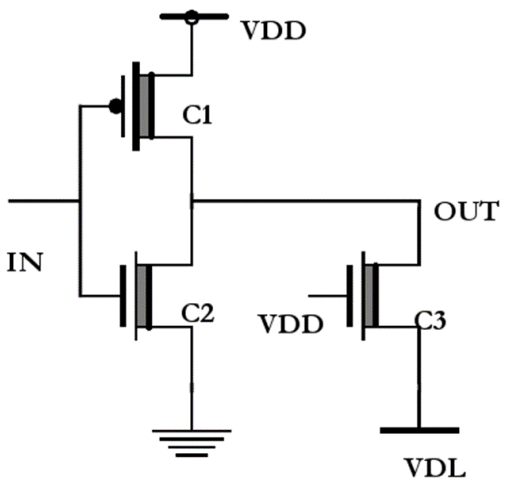

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

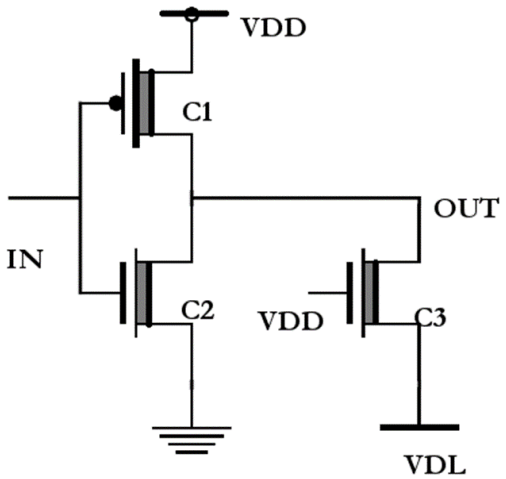

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

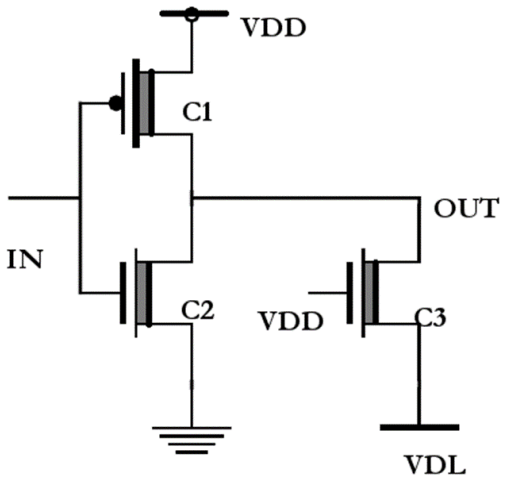

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

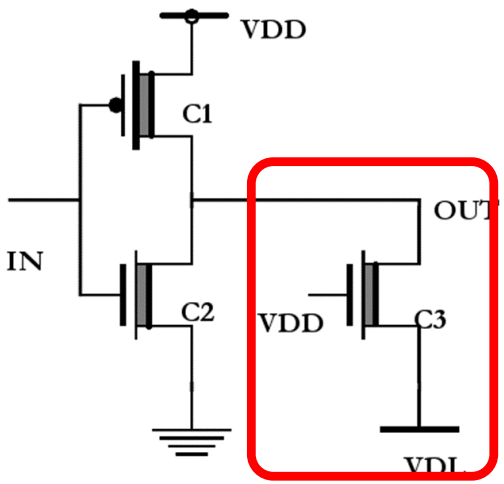

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

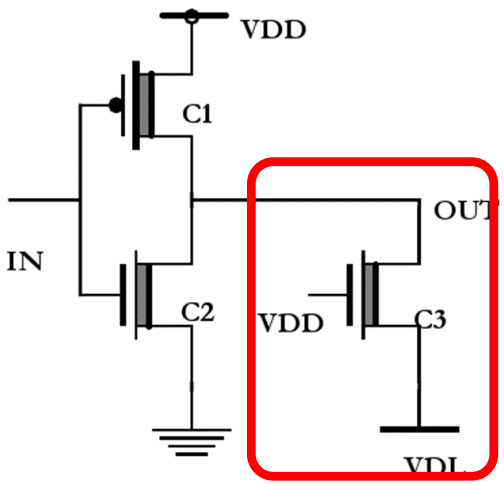

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Standard Ternary Inverter

Key Statement

Improved performance of the inverter of a memory cell leads to **increased performance** of the whole ternary system

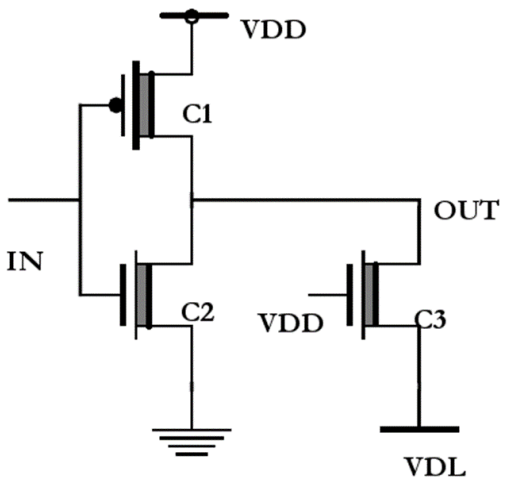

- Primary Building Block for MVL
- Multiple power supplies
- VDD = 0.9 V and VDD = 0.45 V
- Transistor C3 is always ON
- C3 plays a vital role for Intermediate Logic 1 : VDD/2

Characteristics of Ternary SRAM Cell

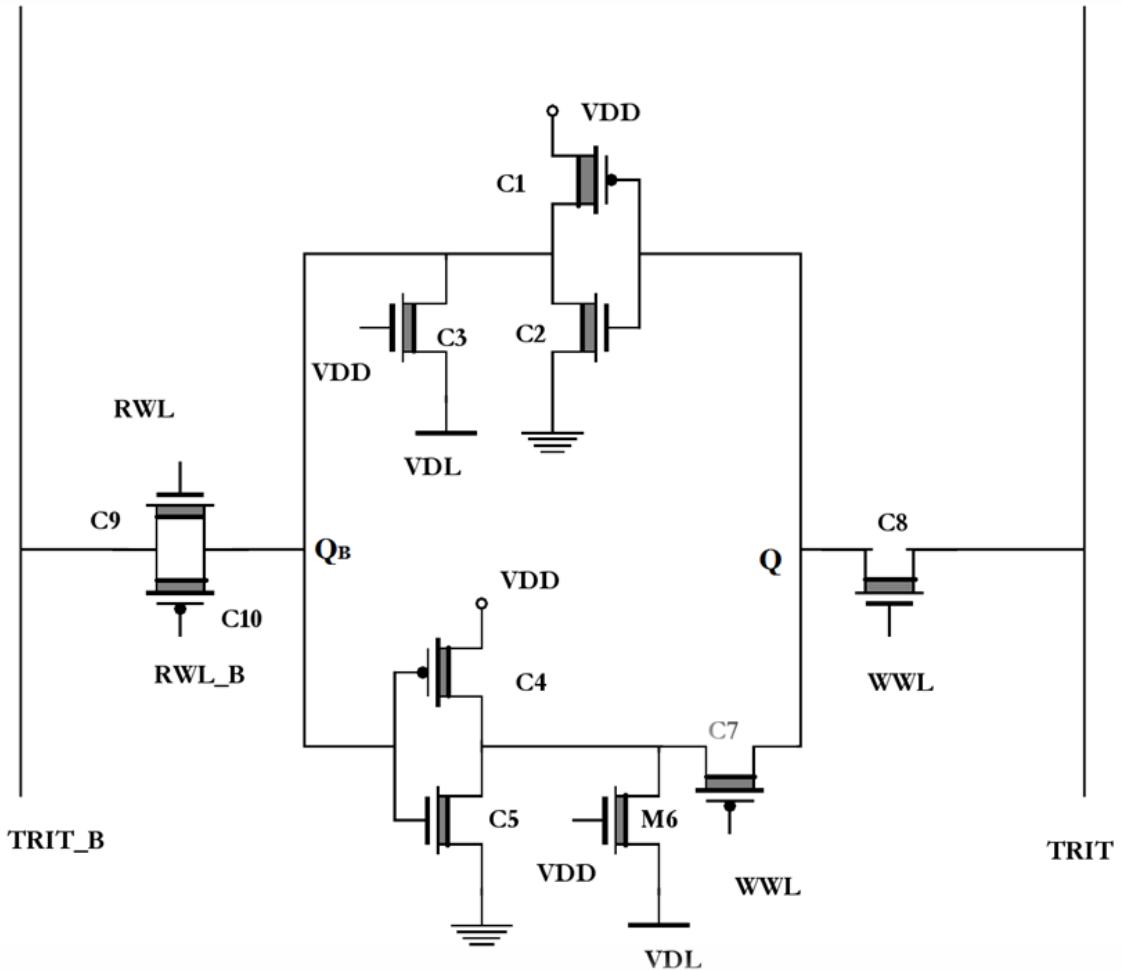

Characteristics of Ternary SRAM Cell

Standard Ternary Inverter

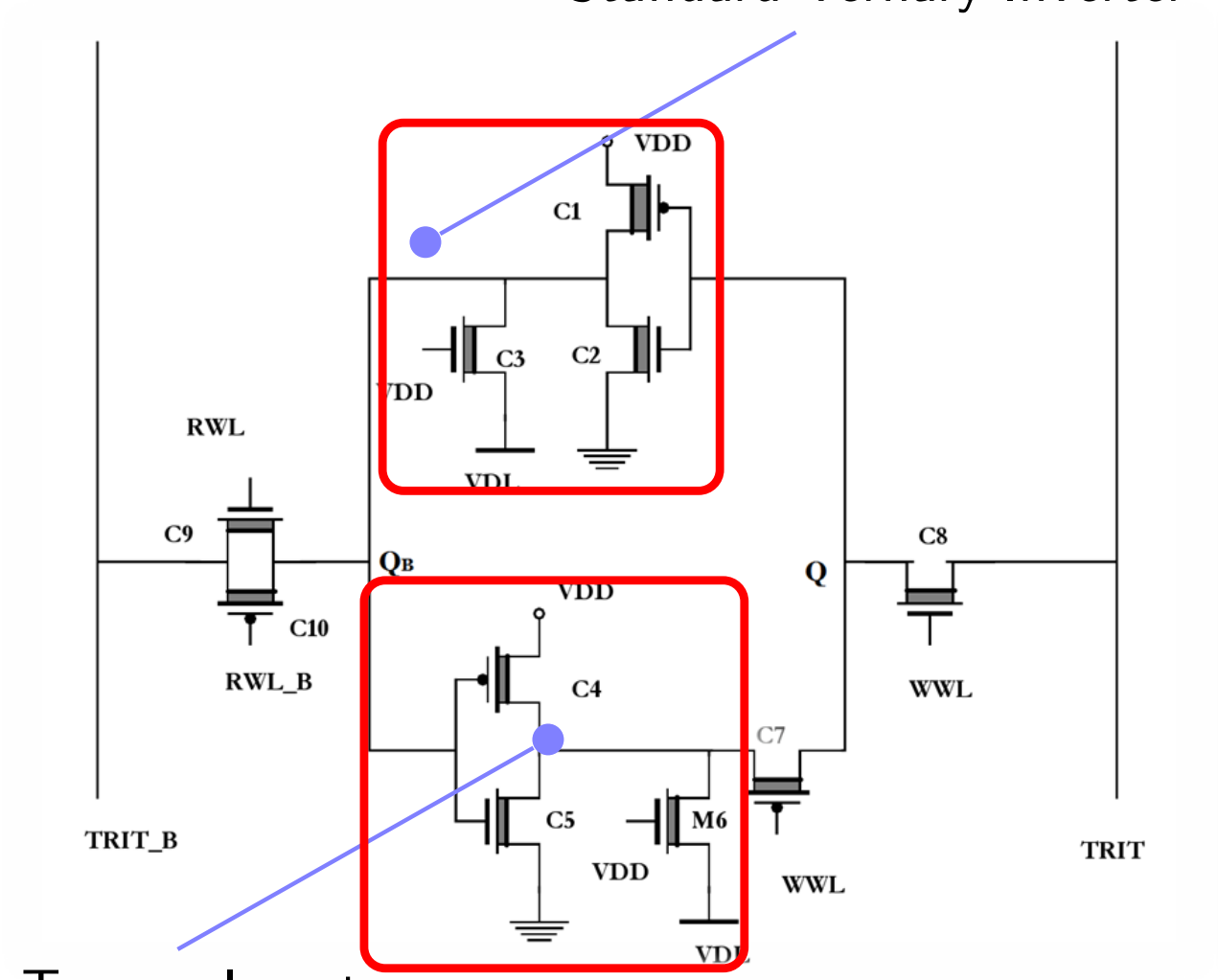

Standard Ternary Inverter

Characteristics of Ternary SRAM Cell

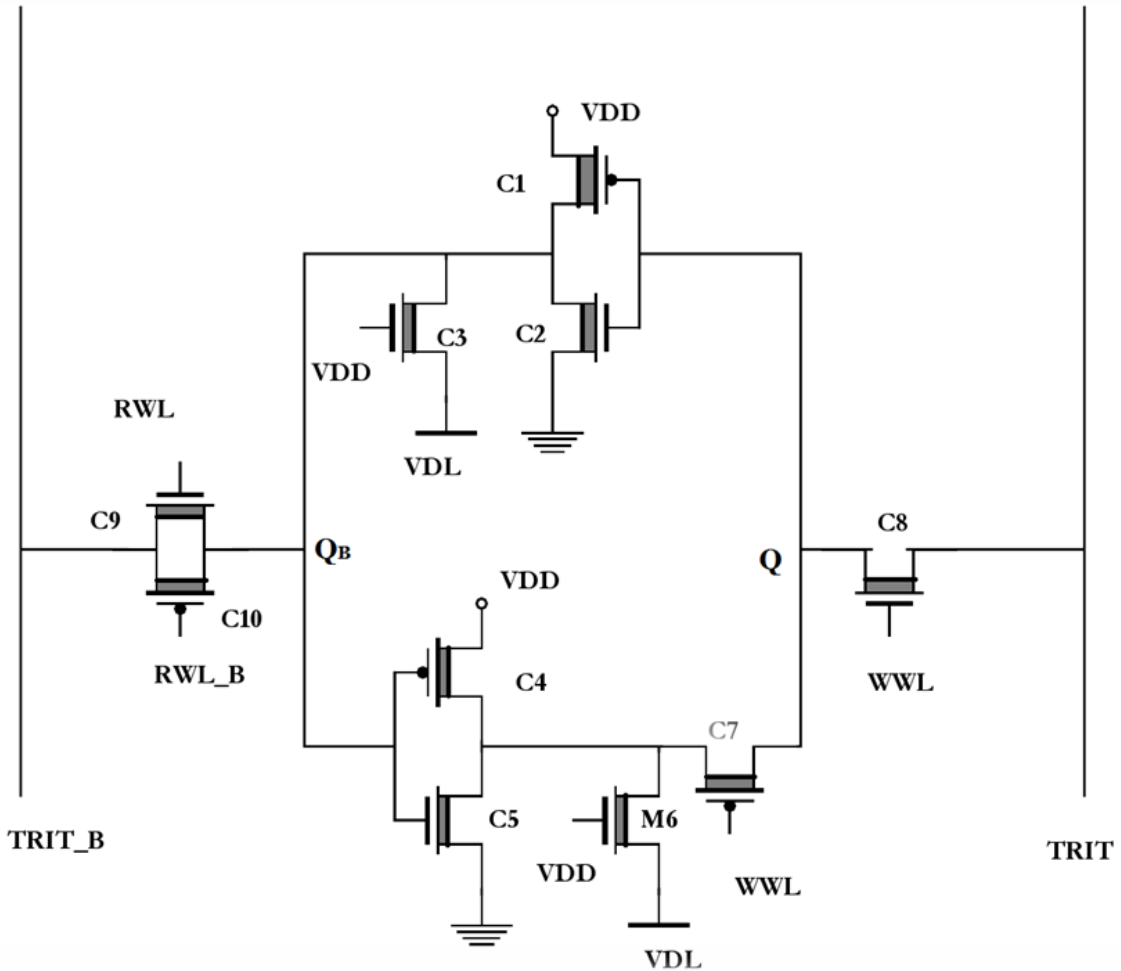

Characteristics of Ternary SRAM Cell

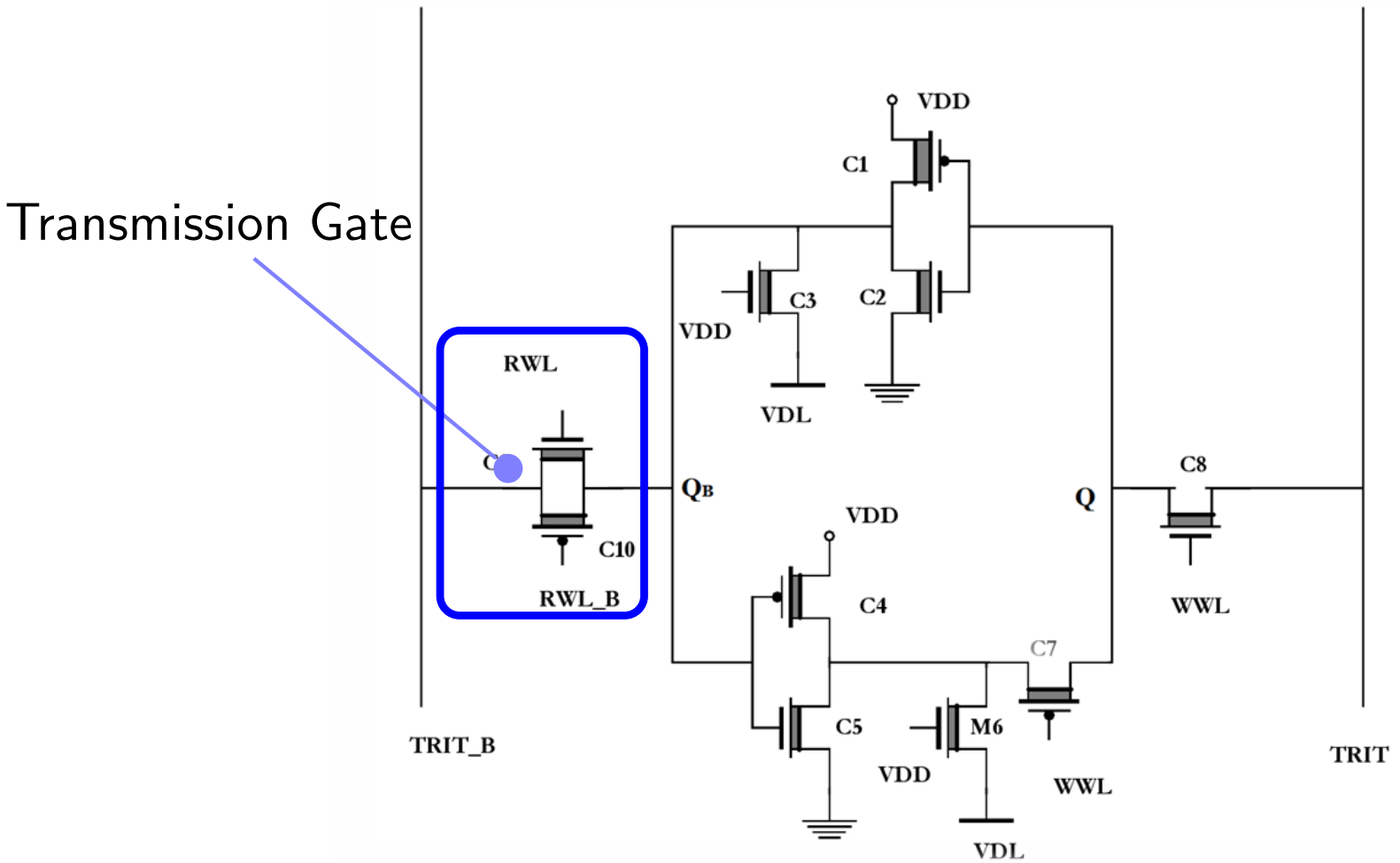

Characteristics of Ternary SRAM Cell

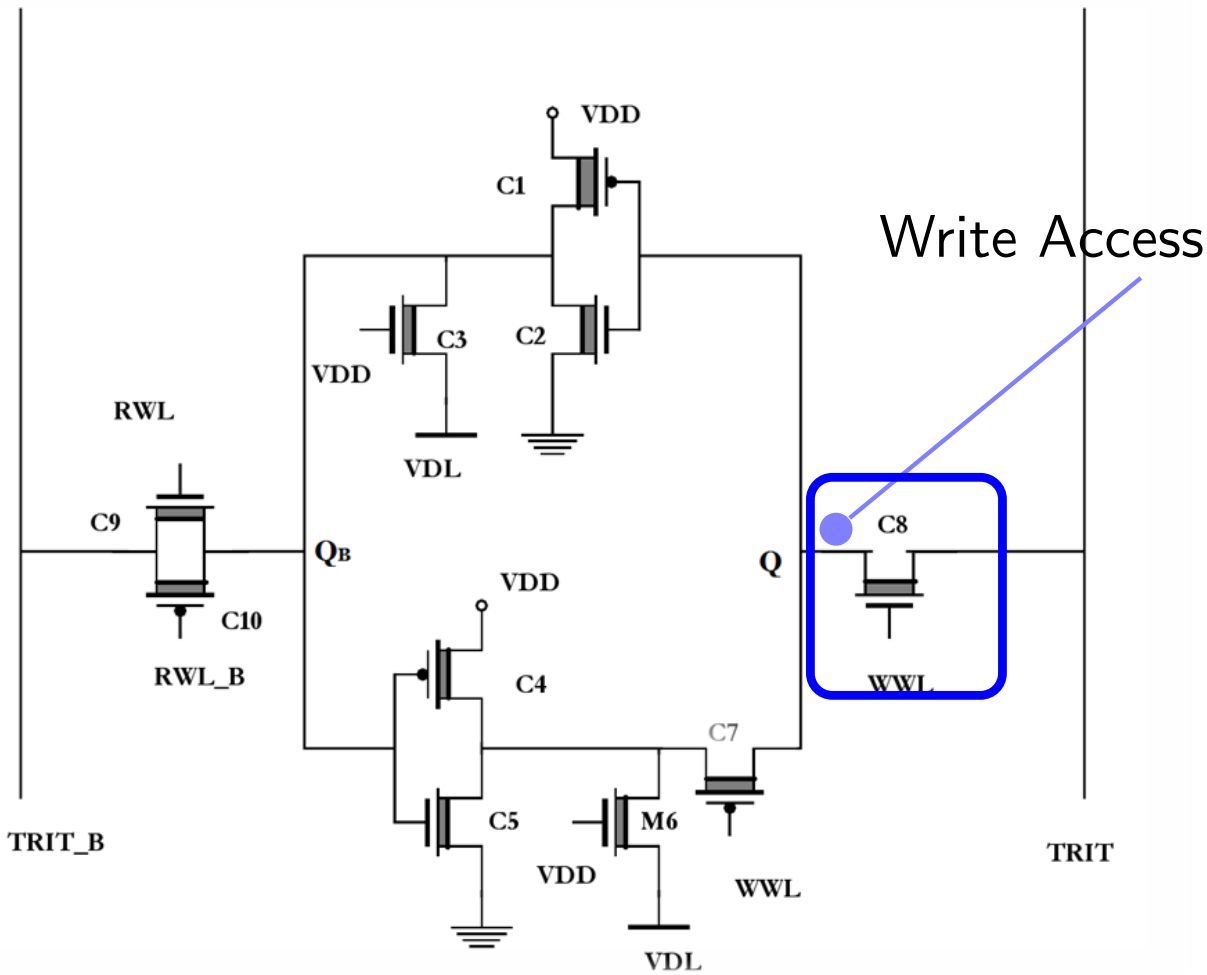

Write Access Transistor

Characteristics of Ternary SRAM Cell

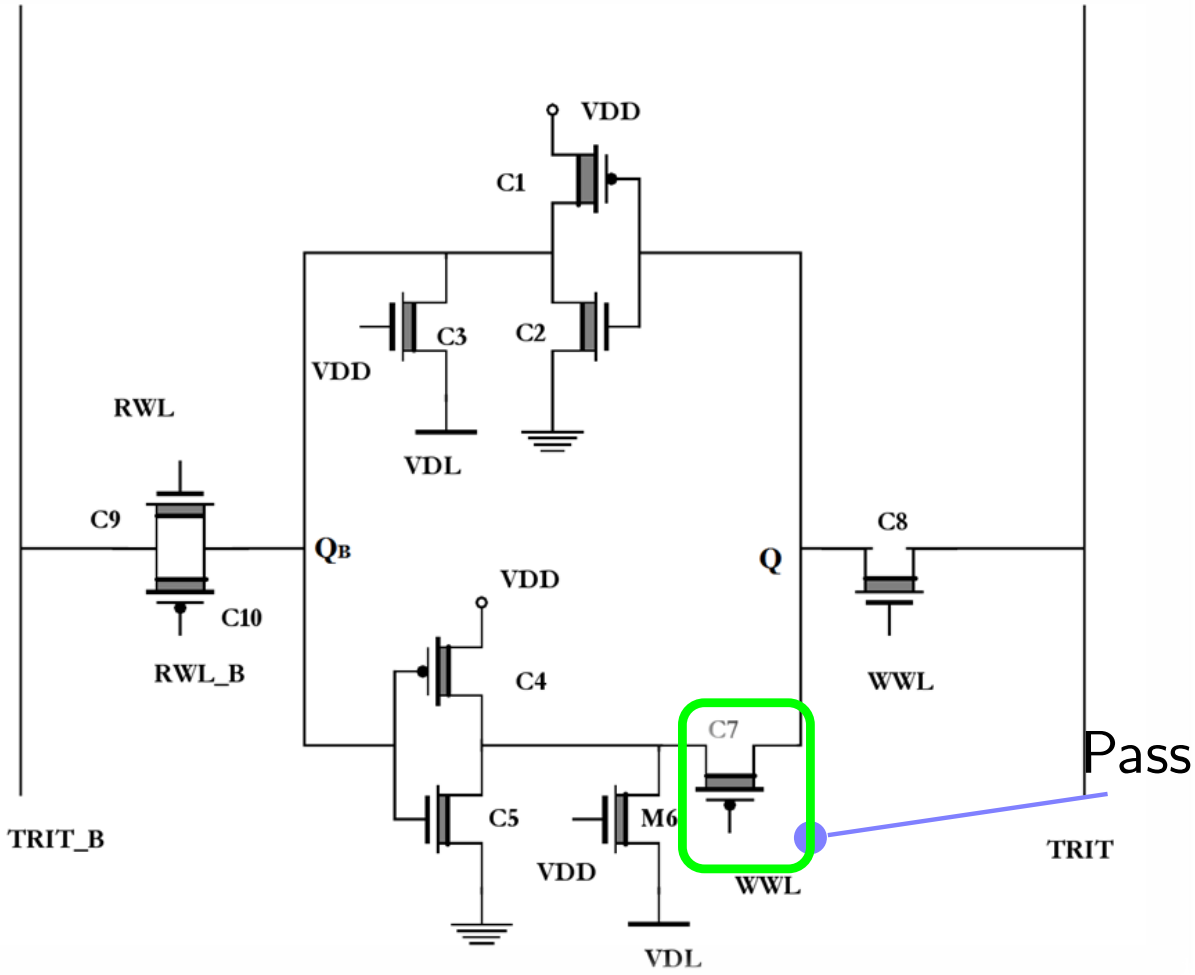

Simulation Environment Setup

- Evaluation is done using Synopsis's HSPICE simulator with 32nm Stanford CNTFET model which includes a number of practical non idealities
- All the designs are simulated at room temperature, 250 MHz operating frequency, 0.9V power supply voltage with output load capacitor of 2.1fF

Read and Write Operations

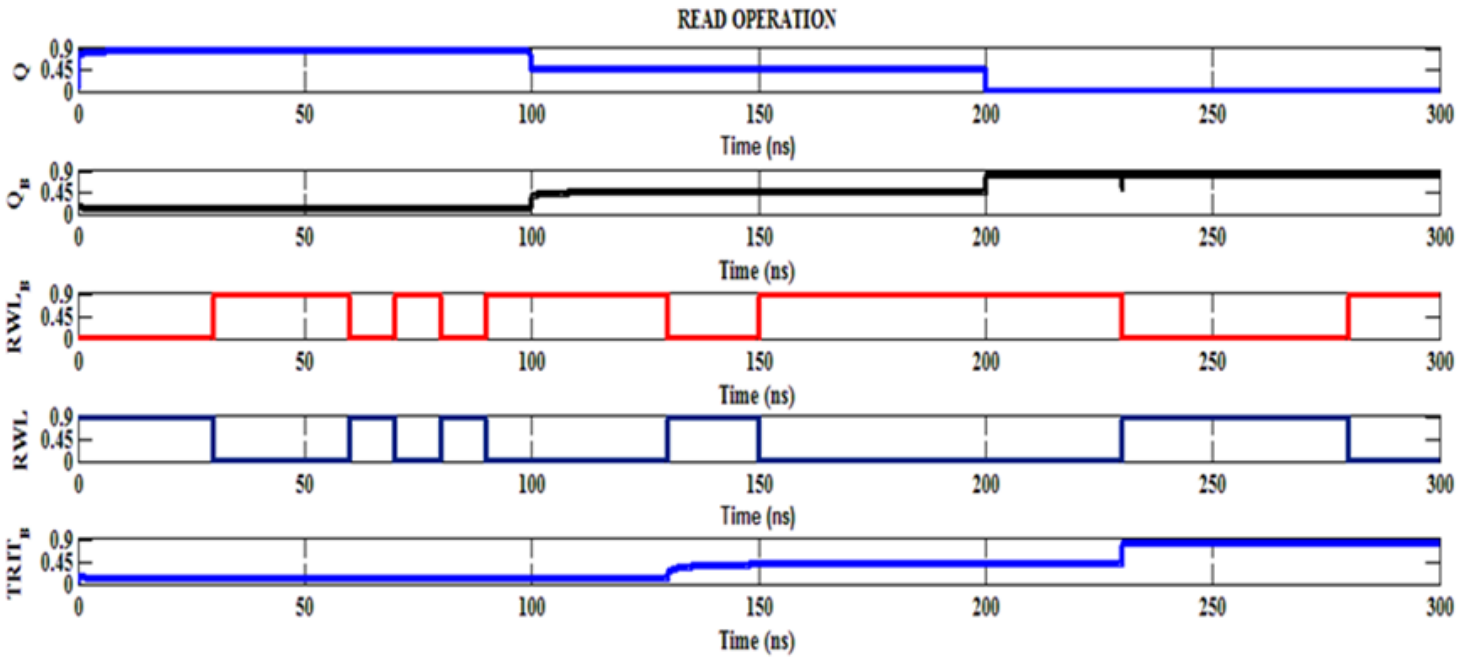

Figur: Read Transient Simulation Result

Read and Write Operations

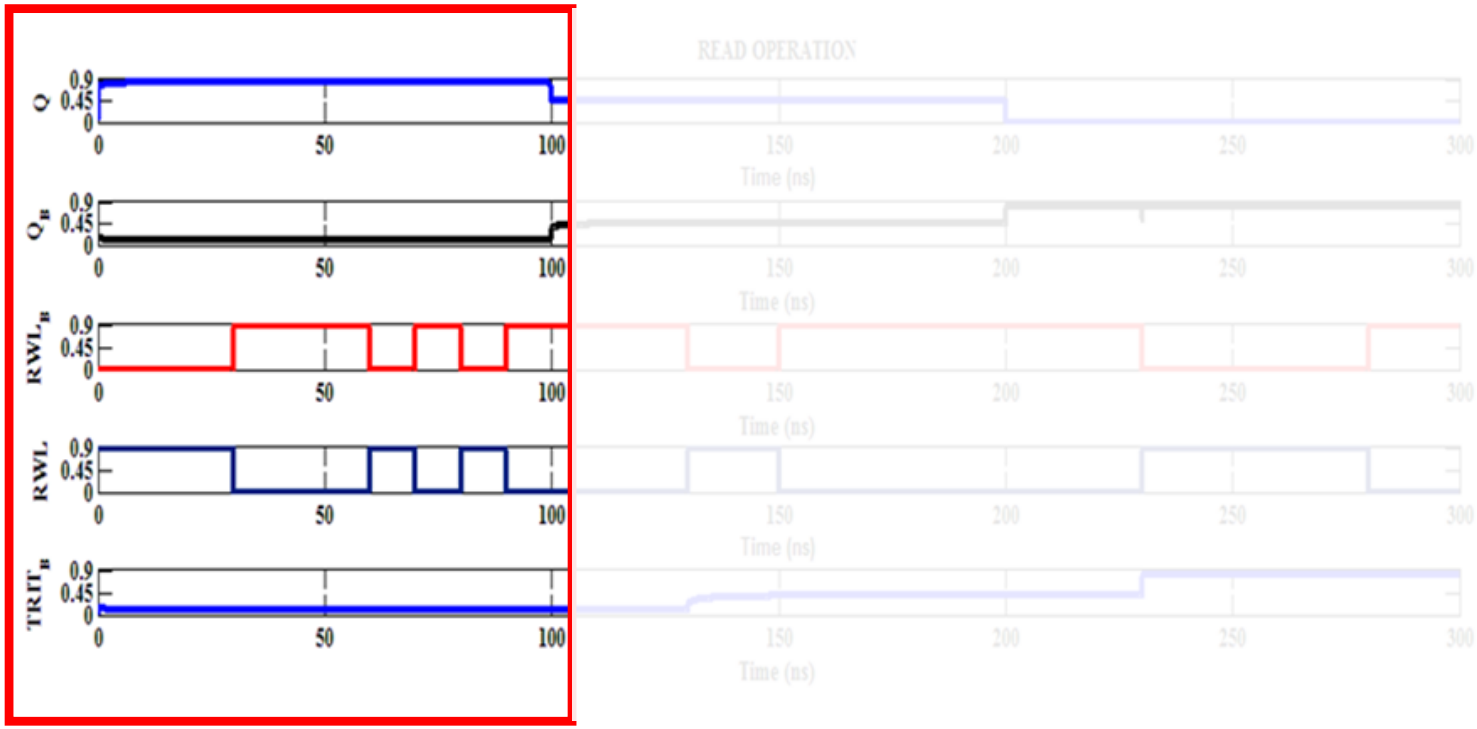

Figur: Read Transient Simulation Result

Read and Write Operations

Figur: Read Transient Simulation Result

Read and Write Operations

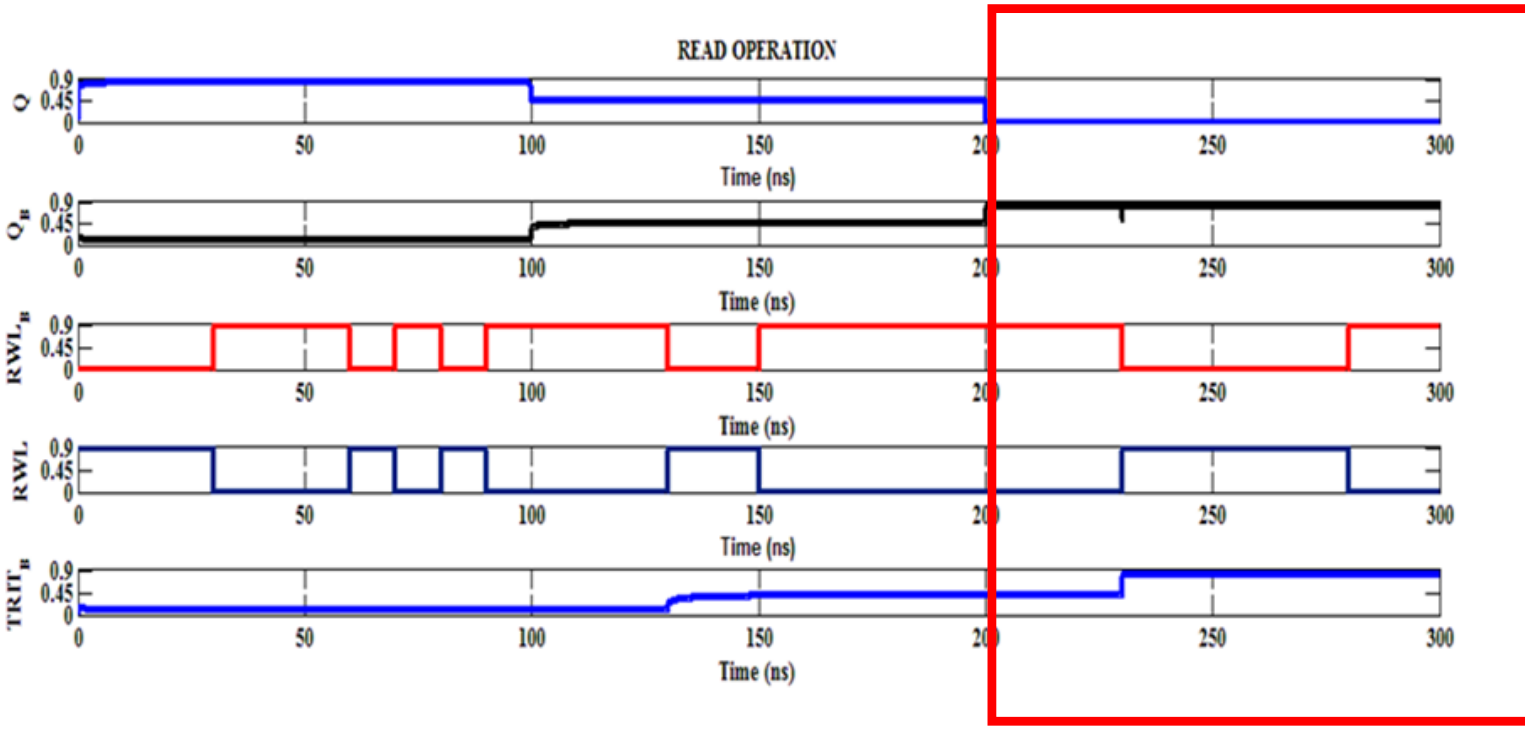

Figur: Read Transient Simulation Result

Read and Write Operations

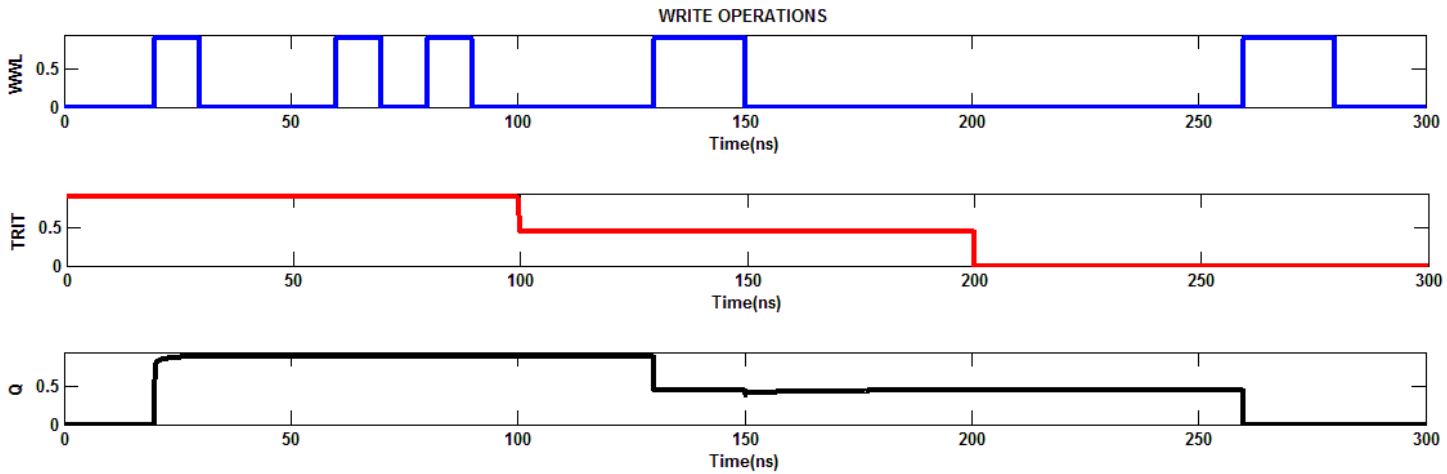

Figur: Read Transient Simulation Result

Read and Write Operations

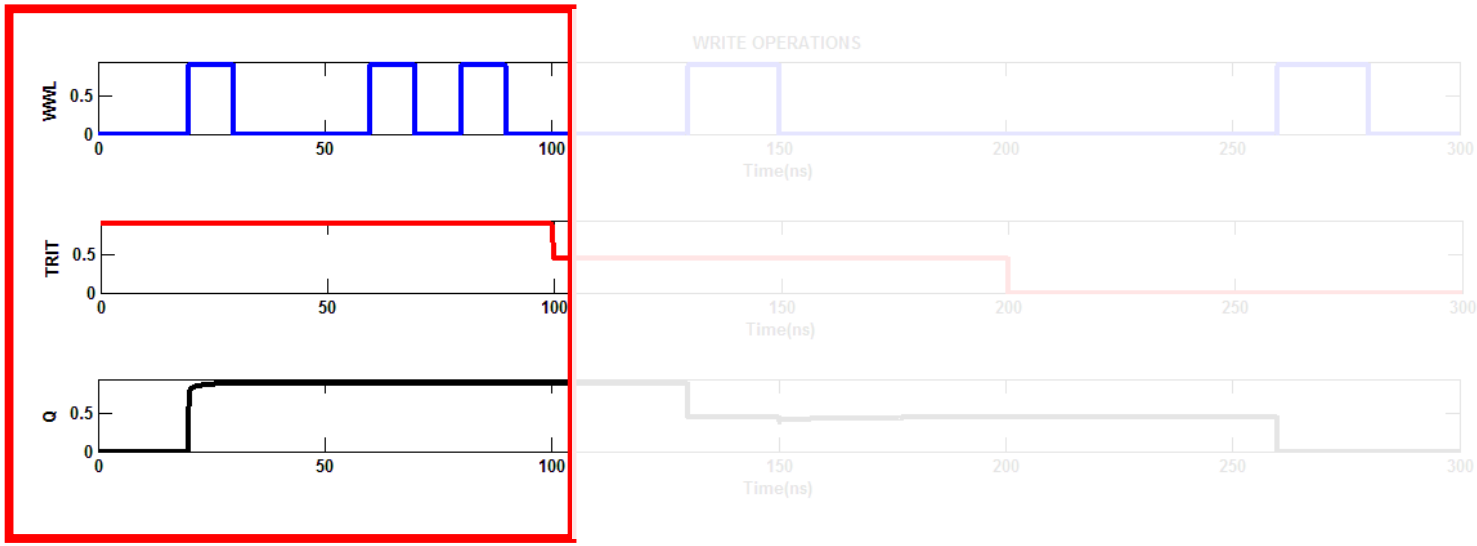

Figur: Read Transient Simulation Result

Read and Write Operations

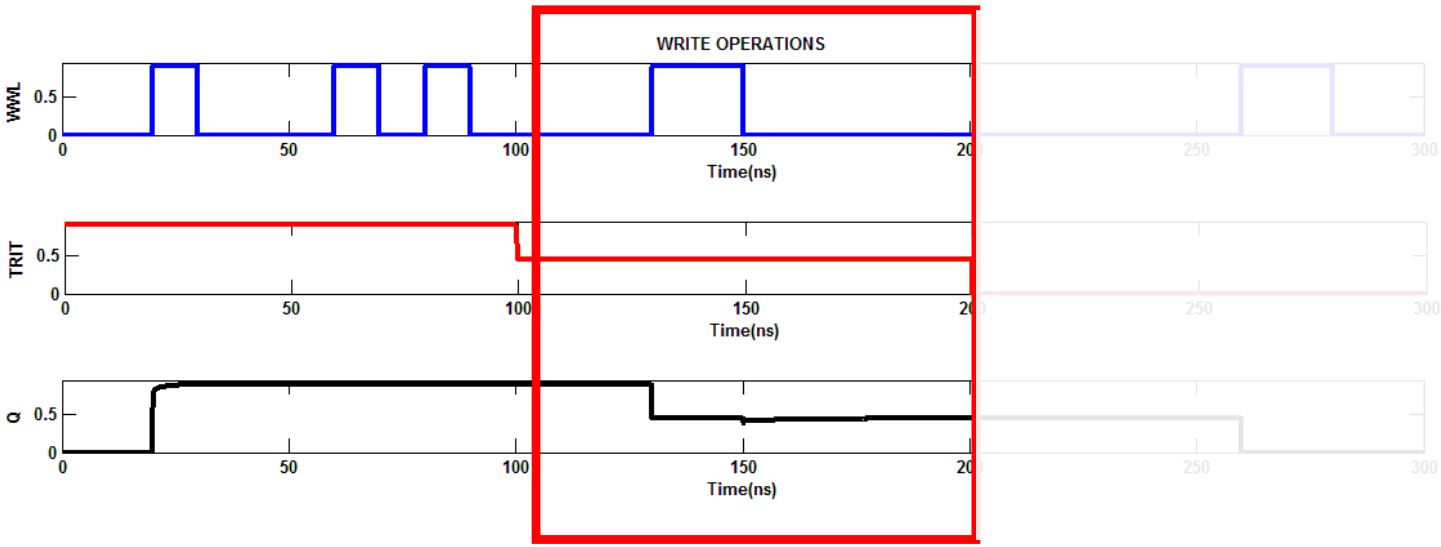

Figur: Read Transient Simulation Result

Read and Write Operations

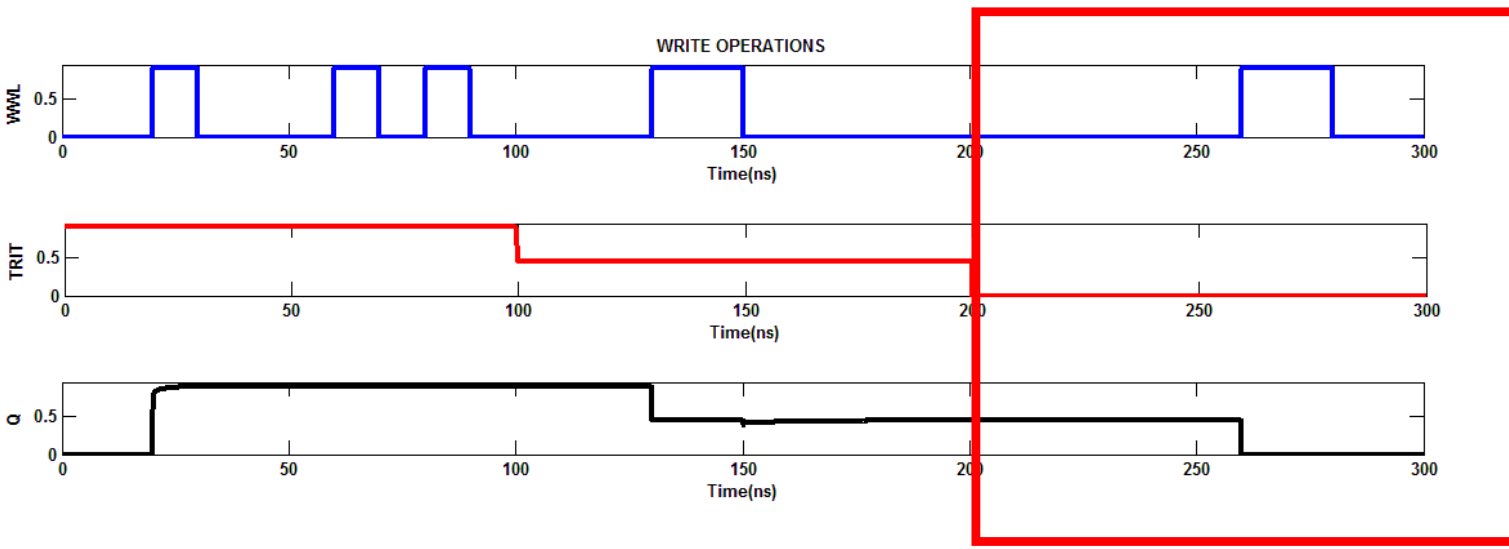

Figur: Read Transient Simulation Result

Simulation Results(contd)

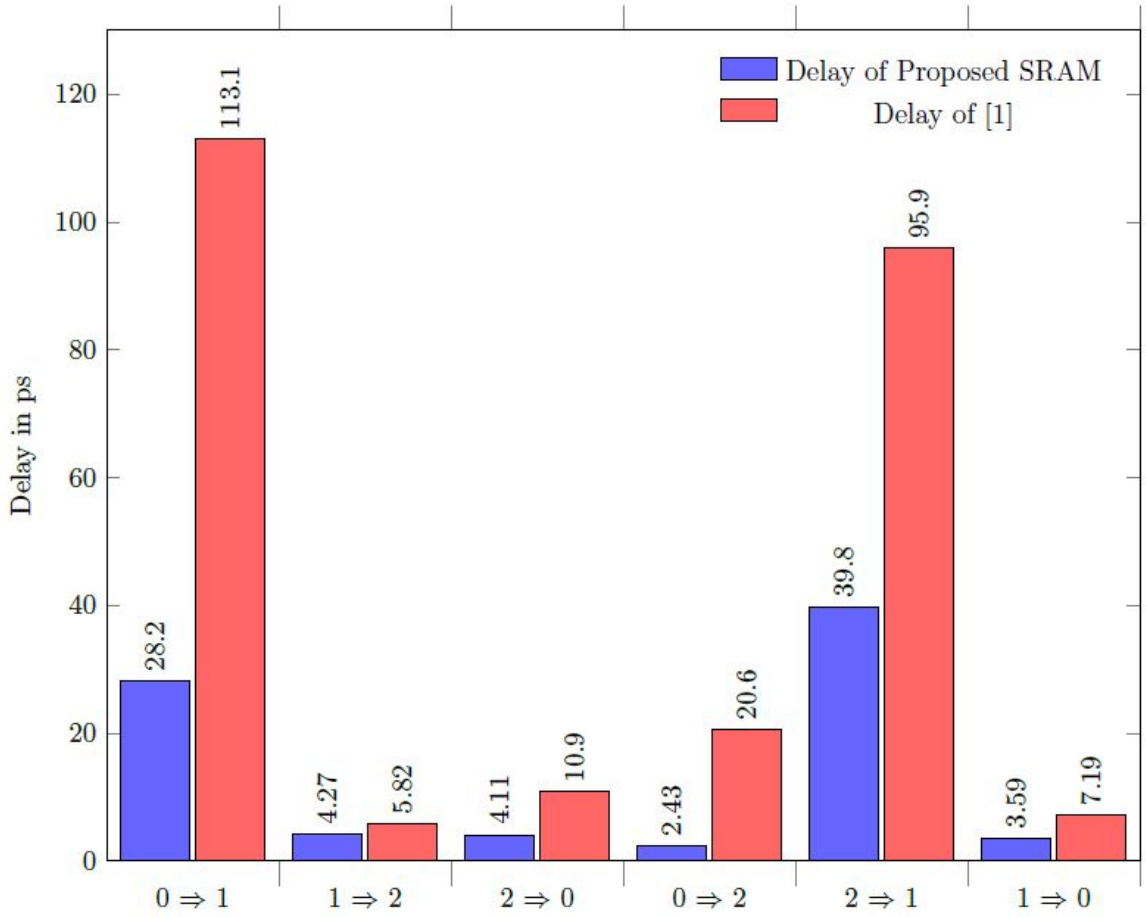

Figur: Comparison of Write Simulation Results

Simulation Results(contd)

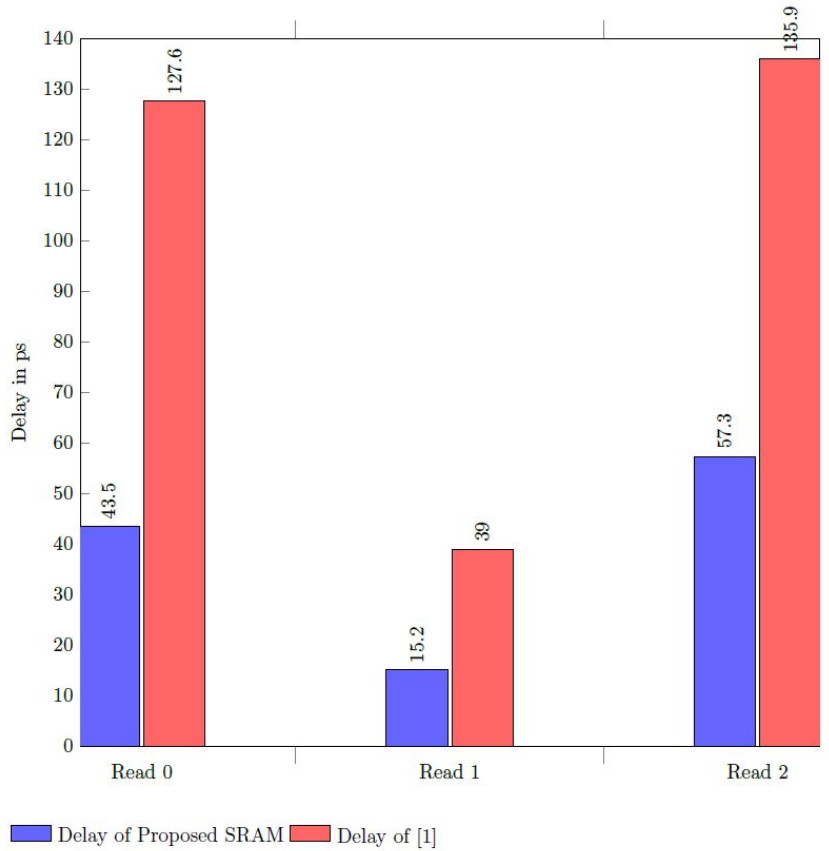

Figur: Comparison of Read Simulation Results

Static Noise Margin

- CNT Diameter has strongest impact.
- Monte Carlo simulations to assess the process variations

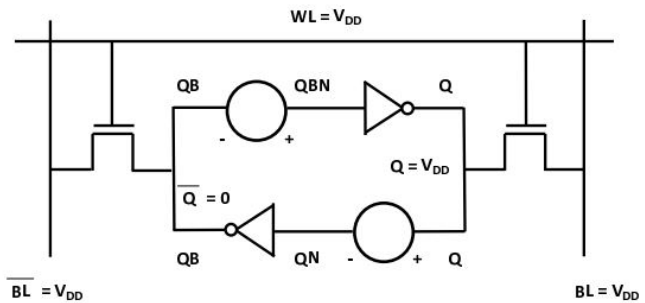

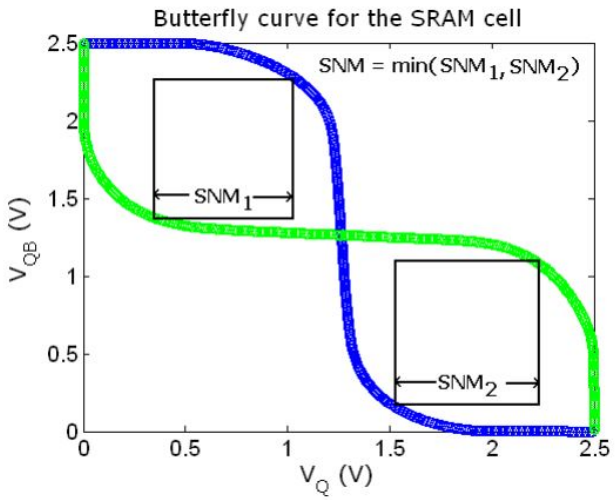

Static Noise Margin

- CNT Diameter has strongest impact.
- Monte Carlo simulations to assess the process variations

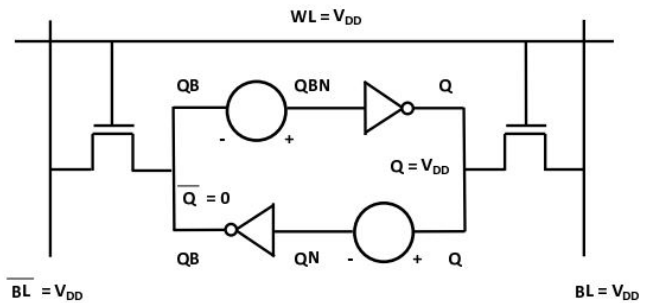

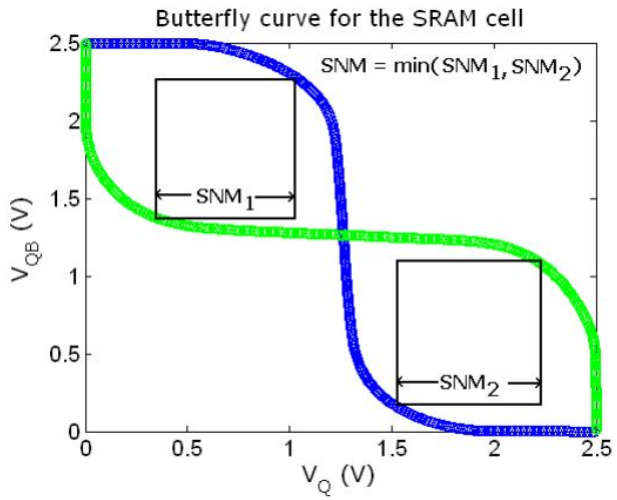

Static Noise Margin

- CNT Diameter has strongest impact.
- Monte Carlo simulations to assess the process variations

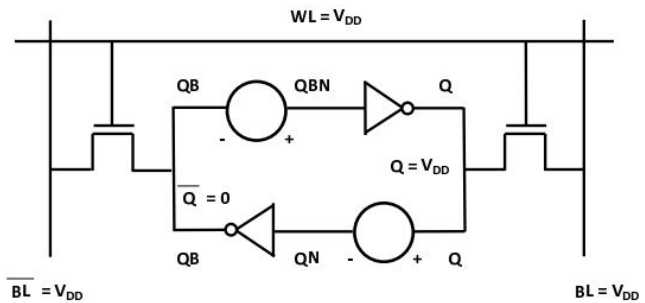

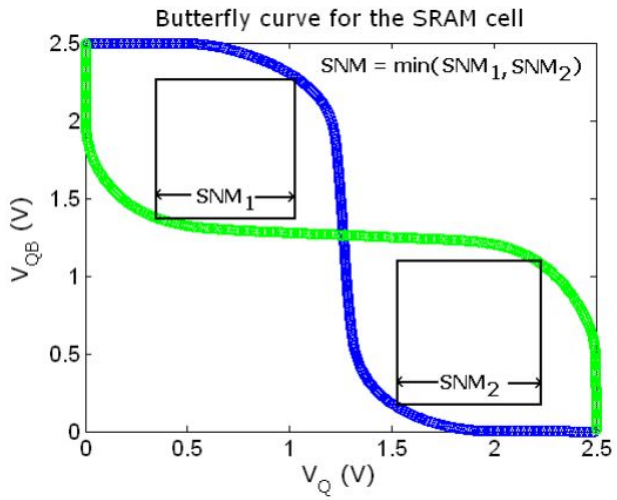

Simulation Results(contd)

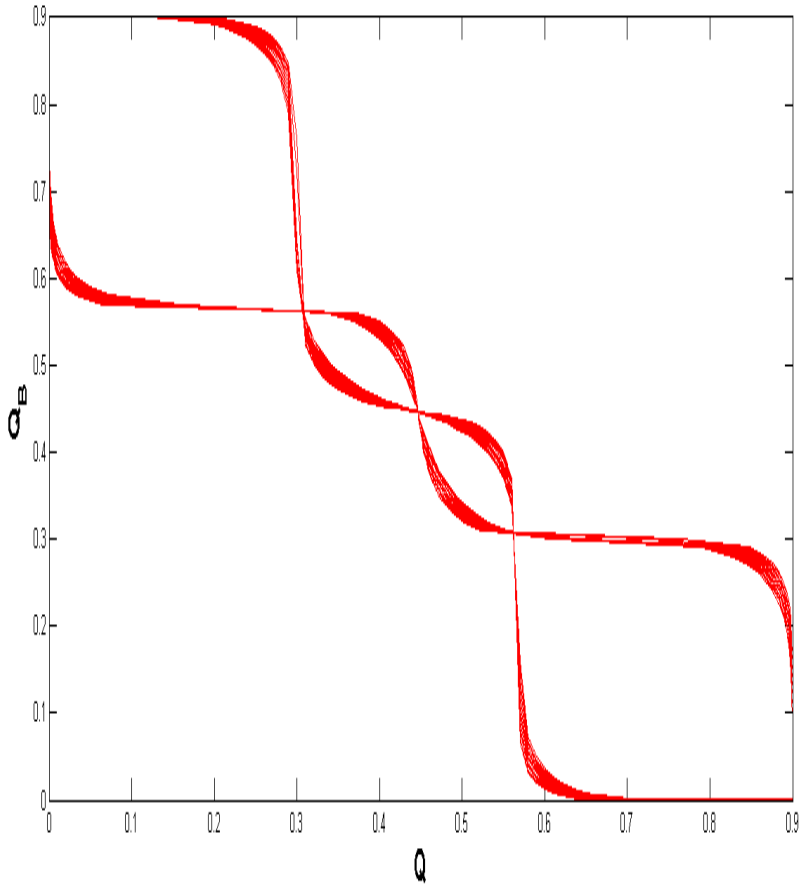

Figur: Static Noise Margin Butterfly Curve under various process variations

Performance Evaluation Parameters

- Cell design using multi-threshold method leveraging the unique characteristics of the CNTFET.
- Proposed memory cell design has one of the lowest number of transistors
- HSPICE simulations have demonstrated the correct functionality with **less area** and **high speed**.
- The SRAM cell outperforms the design proposed in [1] in write and read operations

Thank you

References

1. Lin S., Kim Y.B., Lombardi F. : 'Design of a CNTFET based SRAM cell by dual-chirality selection',*IEEE Trans. Nanotechnology*, 2010, 9,(1), pp. 30-37.
2. K. You, K. Nepal, Design of a ternary static memory cell using carbon nanotube-based transistors, *Published in Micro & Nano Letters*; 4th April 2011.